



The Linter

Project 1: Spartan6 - DSP48A1

Presented For:

Digital Design Using Verilog & FPGA Flow Using Vivado Diploma - V11

Under Supervision of: Eng. Kareem Waseem

Digital Designer

Magdy Ahmed Abbas Abdelhamid




 DSP48A1


 RTL Design

OVERVIEW

Many DSP algorithms are supported with minimal use of the general - purpose FPGA logic, resulting in low power, high performance, and efficient device utilization. At first look, the DSP48A1 slice contains an 18 - bit input pre-adder followed by an 18 x 18 - bit two's complement multiplier and a 48 - bit sign - extended adder/subtractor/accumulator, a function that is widely used in digital signal processing.

A second look reveals many subtle features that enhance the usefulness, versatility, and speed of this arithmetic building block. Programmable pipelining of input operands, intermediate products, and accumulator outputs enhances throughput. The 48 - bit internal bus allows for practically unlimited aggregation of DSP slices.


One of the most important features is the ability to cascade a result from one DSP48A1 slice to the next without the use of general fabric routing. This path provides high - performance and low - power post addition for many DSP filter functions of any tap length.

Another key feature for filter composition is the ability to cascade an input stream from slice to slice.

The C input port allows the formation of many 3 - input mathematical functions, such as 3 - input addition by cascading the pre - adder with the post - adder, and 2 - input multiplication with a single addition.

The D input allows a second argument to be used with the pre - adder to reduce DSP48A1 slice utilization in symmetric filters.

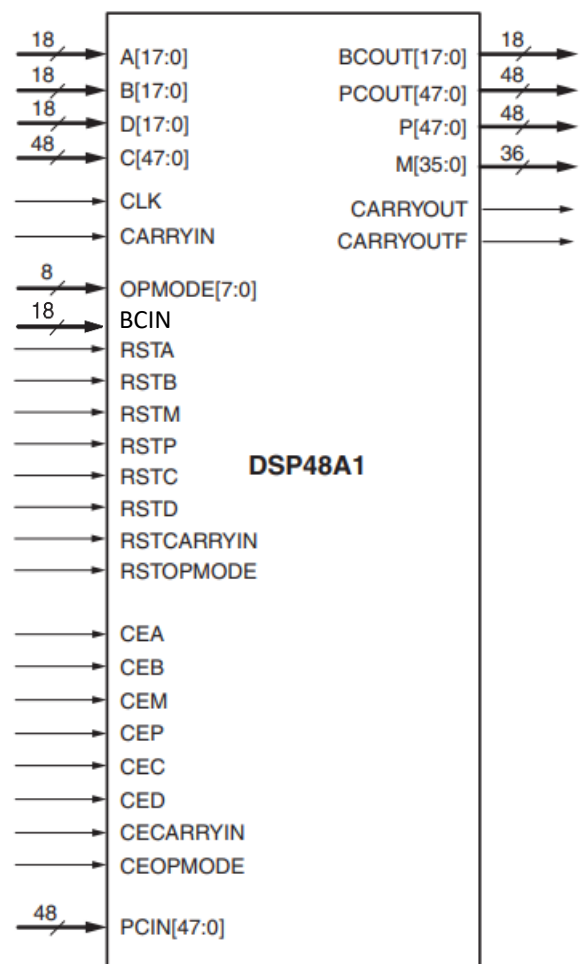
The Spartan - 6 family offers a high ratio of DSP48A1 slices to logic, making it ideal for math-intensive applications.



DSP48A1 SLICE IN DETAIL

The Blue Signals Are Internal Registers

The Red Signals Are internal Wires

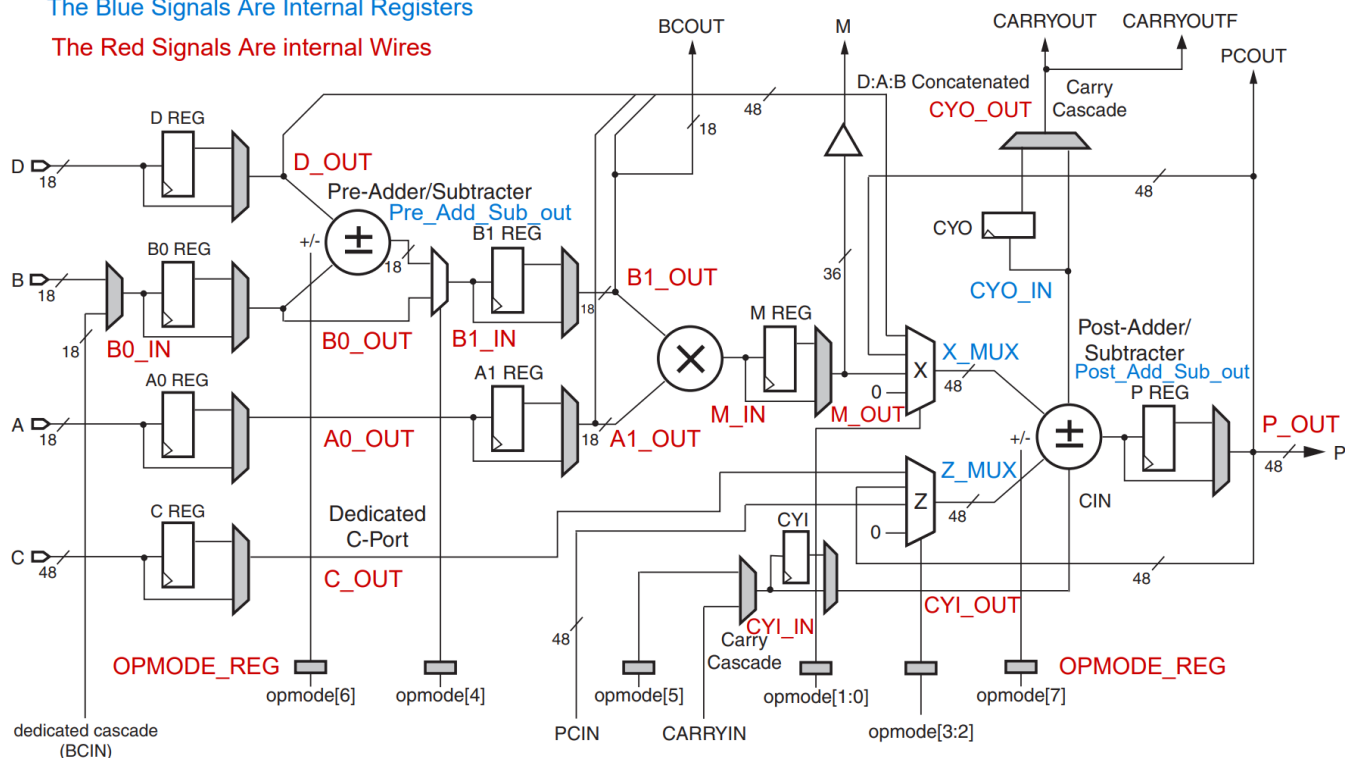

LOWER MODULE

```
module Comb_Seq_MUX (rst, clk, CE, in, out);
```

```
// Instanstiation
```

```
// Comb_Seq_MUX #(WIDTH(),.RSTTYPE(),.Sel_REG()) Name (.rst(),.clk(),.CE(),.in(),.out());
```

```
parameter WIDTH = 18;
```

```
parameter RSTTYPE = "SYNC";
```

```
parameter Sel_REG = 0; // Selection of the MUX
```

```
input rst, clk, CE; // CE stands for Clock Enable
```

```
input [WIDTH - 1 : 0] in;
```

```
output [WIDTH - 1 : 0] out;
```

```
reg [WIDTH - 1 : 0] OUT_Seq;
```


```

generate // Sequential Flip – Flop
  if (RSTTYPE == "SYNC") begin
    always @(posedge clk) begin
      if (rst)
        OUT_Seq <= 0;
      else
        if (CE)
          OUT_Seq <= in;
    end
  end
else
  if (RSTTYPE == "ASYNC") begin
    always @(posedge clk or posedge rst) begin
      if (rst)
        OUT_Seq <= 0;
      else
        if (CE)
          OUT_Seq <= in;
    end
  end
endgenerate

// If Sel_REG = 1 -> Sequential Flip – Flop , Sel_REG = 0 -> Combinational
assign out = (Sel_REG)? OUT_Seq : in;

endmodule

```

 

TOP MAIN MODULE

```

module DSP48A1
(A, B, D, C, CLK, CARRYIN, OPMODE, BCIN, RSTA, RSTB, RSTM, RSTP, RSTC, RSTD, RSTCARRYIN, RSTOPMODE,
CEA, CEB, CEM, CEP, CEC, CED, CECARRYIN, CEOPMODE, PCIN, BCOUT, PCOUT, P, M, CARRYOUT, CARRYOUTF);

// All Input Ports Declaration
input [17:0] A, B, D, BCIN;
input [47:0] C, PCIN;
input CLK, CARRYIN, RSTA, RSTB, RSTM, RSTP, RSTC, RSTD, RSTCARRYIN, RSTOPMODE;
input CEA, CEB, CEM, CEP, CEC, CED, CECARRYIN, CEOPMODE;
input [7:0] OPMODE;

// All Output Ports Declaration
output [17:0] BCOUT;
output [47:0] PCOUT, P;
output [35:0] M;
output CARRYOUT, CARRYOUTF;

// All Parameters Declaration
parameter A0REG = 0; // No Register
parameter A1REG = 1; // Registered
parameter B0REG = 0; // No Register
parameter B1REG = 1; // Registered
parameter CREG = 1; // Registered
parameter DREG = 1; // Registered
parameter MREG = 1; // Registered
parameter PREG = 1; // Registered
parameter CARRYINREG = 1; // Registered
parameter CARRYOUTREG = 1; // Registered
parameter OPMODEREG = 1; // Registered
parameter CARRYINSEL = "OPMODE5"; // May be OPMODE5 or CARRYIN or no of them -> 0
parameter B_INPUT = "DIRECT"; // May be (DIRECT -> B Port, CASCADE -> BCIN, no of them -> 0)
parameter RSTTYPE = SYNC;
// May be "SYNC" Stands for SYNChronous or "ASYN" Stands for ASYNChronous

// All Internal Wires And Regs Declaration
wire [17:0] D_OUT, B0_IN, B0_OUT, A0_OUT, B1_IN, B1_OUT, A1_OUT;
wire [47:0] C_OUT, P_OUT;
wire [35:0] M_IN, M_OUT;
wire CYI_IN, CYI_OUT, CYO_OUT;
wire [7:0] OPMODE_REG;
reg CYO_IN;
reg [47:0] Post_Add_Sub_out;
reg [17:0] Pre_Add_Sub_out;
reg [47:0] X_MUX, Z_MUX;

```

```

// Make Instantiations for Registers From Comb_Seq_MUX Module
Comb_Seq_MUX #(. WIDTH(18),. RSTTYPE(RSTTYPE),. Sel_REG(DREG))
D_REG(. rst(RSTD),. clk(CLK),. CE(CED),. in(D),. out(D_OUT));
Comb_Seq_MUX #(. WIDTH(18),. RSTTYPE(RSTTYPE),. Sel_REG(B0REG))
B0_REG(. rst(RSTB),. clk(CLK),. CE(CEB),. in(B0_IN),. out(B0_OUT));
Comb_Seq_MUX #(. WIDTH(18),. RSTTYPE(RSTTYPE),. Sel_REG(A0REG))
A0_REG(. rst(RSTA),. clk(CLK),. CE(CEA),. in(A),. out(A0_OUT));
Comb_Seq_MUX #(. WIDTH(48),. RSTTYPE(RSTTYPE),. Sel_REG(CREG))
C_REG(. rst(RSTC),. clk(CLK),. CE(CEC),. in(C),. out(C_OUT));
Comb_Seq_MUX #(. WIDTH(18),. RSTTYPE(RSTTYPE),. Sel_REG(B1REG))
B1_REG(. rst(RSTB),. clk(CLK),. CE(CEB),. in(B1_IN),. out(B1_OUT));
Comb_Seq_MUX #(. WIDTH(18),. RSTTYPE(RSTTYPE),. Sel_REG(A1REG))
A1_REG(. rst(RSTA),. clk(CLK),. CE(CEA),. in(A0_OUT),. out(A1_OUT));
Comb_Seq_MUX #(. WIDTH(36),. RSTTYPE(RSTTYPE),. Sel_REG(MREG))
M_REG(. rst(RSTM),. clk(CLK),. CE(CEM),. in(M_IN),. out(M_OUT));
Comb_Seq_MUX #(. WIDTH(1),. RSTTYPE(RSTTYPE),. Sel_REG(CARRYINREG))
CARRYIN_REG(. rst(RSTCARRYIN),. clk(CLK),. CE(CECARRYIN),. in(CYI_IN),. out(CYI_OUT));
Comb_Seq_MUX #(. WIDTH(1),. RSTTYPE(RSTTYPE),. Sel_REG(CARRYOUTREG))
CARRYOUT_REG(. rst(RSTCARRYIN),. clk(CLK),. CE(CECARRYIN),. in(CYO_IN),. out(CYO_OUT));
Comb_Seq_MUX #(. WIDTH(48),. RSTTYPE(RSTTYPE),. Sel_REG(PREG))
P_REG(. rst(RSTP),. clk(CLK),. CE(CEP),. in(Post_Add_Sub_out),. out(P_OUT));
Comb_Seq_MUX #(. WIDTH(8),. RSTTYPE(RSTTYPE),. Sel_REG(OPMODEREG))
Opmode_REG(. rst(RSTOPMODE),. clk(CLK),. CE(CEOPMODE),. in(OPMODE),. out(OPMODE_REG));

// Input Wires Assignments
// MUX Check the B_INPUT Parameter
assign B0_IN = (B_INPUT == "DIRECT")? B : (B_INPUT == "CASCADE")? BCIN : 0;
// MUX Check the CARRYINSEL Parameter
assign CYI_IN = (CARRYINSEL == "OPMODE5")? OPMODE_REG[5] : (CARRYINSEL == "CARRYIN")? CARRYIN 0;

// Pre_MUX Check B1_IN of OPMODE_REG[4]
assign B1_IN = (OPMODE_REG[4])? Pre_Add_Sub_out : B0_OUT;
assign M_IN = B1_OUT * A1_OUT; // Multiplier Output

// Check OPMODE_REG[6]
always @(*) begin
    if (OPMODE_REG[6])
        Pre_Add_Sub_out = D_OUT - B0_OUT;
    else
        Pre_Add_Sub_out = D_OUT + B0_OUT;
end

// Check {OPMODE_REG[3], OPMODE_REG[2]}
always @(*) begin
    case ({OPMODE_REG[3], OPMODE_REG[2]})
        2'b00 : Z_MUX = 0;
        2'b01 : Z_MUX = PCIN;
        2'b10 : Z_MUX = P_OUT;
        2'b11 : Z_MUX = C_OUT;
    endcase
end

```

```
// Check {OPMODE_REG[1],OPMODE_REG[0]}
always @(*) begin
    case ({OPMODE_REG[1],OPMODE_REG[0]})
        2'b00 : X_MUX = 0;
        2'b01 : X_MUX = {{12{M_OUT[35]}},M_OUT}; // Sign Extention
        2'b10 : X_MUX = P_OUT;
        2'b11 : X_MUX = {D_OUT[11:0],A1_OUT,B1_OUT};
    endcase
end

// Check OPMODE_REG[7]
always @(*) begin
    if (OPMODE_REG[7])
        {CYO_IN,Post_Add_Sub_out} = Z_MUX - (X_MUX + CYI_OUT);
    else
        {CYO_IN,Post_Add_Sub_out} = Z_MUX + X_MUX + CYI_OUT;
end

// Outputs Assignments (Duplicated and Cascaded Signals Assignment)
assign P = P_OUT;
assign PCOUT = P_OUT;
assign CARRYOUT = CYO_OUT;
assign CARRYOUTF = CYO_OUT;
assign BCOUT = B1_OUT;
assign M = ~(~M_OUT); // buf(M,M_OUT);

endmodule
```

TESTBENCH

```
module DSP48A1_tb ();

// All Input Ports Declaration
reg [17:0] A,B,D,BCIN;
reg [47:0] C,PCIN;
reg CLK,CARRYIN,RSTA,RSTB,RSTM,RSTP,RSTC,RSTD,RSTCARRYIN,RSTOPMODE;
reg CEA,CEB,CEM,CEP,CEC,CED,CECARRYIN,CEOPMODE;
reg [7:0] OPMODE;

// All Output Ports Declaration
wire [17:0] BCOUT;
wire [47:0] PCOUT,P;
wire [35:0] M;
wire CARRYOUT,CARRYOUTF;
```

```

// All Parameters Declaration
parameter AOREG = 0; // No Register
parameter A1REG = 1; // Registered
parameter BOREG = 0; // No Register
parameter B1REG = 1; // Registered
parameter CREG = 1; // Registered
parameter DREG = 1; // Registered
parameter MREG = 1; // Registered
parameter PREG = 1; // Registered
parameter CARRYINREG = 1; // Registered
parameter CARRYOUTREG = 1; // Registered
parameter OPMODEREG = 1; // Registered
parameter CARRYINSEL = "OPMODE5"; // May be OPMODE5 or CARRYIN or no of them -> 0
parameter B_INPUT = "DIRECT"; // May be (DIRECT -> B Port, CASCADE -> BCIN, no of them -> 0)
parameter RSTTYPE = "SYNC"; // May be "SYNC" Stands for SYNChronous or "ASYNC" Stands for ASYNChronous

DSP48A1 #(AOREG,A1REG,BOREG,B1REG,CREG,DREG,MREG,PREG,CARRYINREG,CARRYOUTREG,
OPMODEREG,CARRYINSEL,B_INPUT,RSTTYPE)
DUT (A,B,D,C,CLK,CARRYIN,OPMODE,BCIN,RSTA,RSTB,RSTM,RSTP,RSTC,RSTD,RSTCARRYIN,RSTOPMODE,
CEA,CEB,CEM,CEP,CEC,CED,CECARRYIN,CEOPMODE,PCIN,BCOUT,PCOUT,P,M,CARRYOUT,CARRYOUTF);

// To Test At The End of the Operation
                                M_Flag = 1 and then Compare Between M & M_REF & Test the Other Outputs

integer Flag = 0;

// For Testing M REG & Also BCOUT
reg [35:0] M_REF;

// Clock Generation
initial begin
    CLK = 0;
    forever
        #1 CLK = ~CLK; // This Means that Clock Period = 2 ns
end

// Testing For All Outputs
initial begin
    // Initialization
    A = 0; B = 0; C = 0; D = 0; PCIN = 0; BCIN = 0; CARRYIN = 0; OPMODE = 0;
    // Active High All The Clock Enables for All Inputs to Sample The Input of The Flip – Flops
    CEA = 1; CEB = 1; CEC = 1; CED = 1; CEM = 1; CEP = 1; CEOPMODE = 1; CECARRYIN = 1;
    // Initially Reset the Circuit for 10 Cycles
    RSTA = 1; RSTB = 1; RSTC = 1; RSTD = 1; RSTM = 1; RSTP = 1; RSTCARRYIN = 1;
                                RSTOPMODE = 1;

    repeat (10) @(negedge CLK);
    RSTA = 0; RSTB = 0; RSTC = 0; RSTD = 0; RSTM = 0; RSTP = 0; RSTCARRYIN = 0;
                                RSTOPMODE = 0;

    // As We Know That All Outputs Will Be Ready After Delay of Few Clock Cycles
                                For Example (P & PCOUT) Will Be Ready After 5 CLK Cycles
    repeat (5) @(negedge CLK);

```



```

@(negedge CLK);
// Testing for 20 iteration
repeat (20) begin
    #10;
    A = $urandom_range(0,1000);
    B = $urandom_range(0,1000);
    C = $urandom_range(0,1000);
    D = $urandom_range(0,1000);
    PCIN = $urandom_range(0,1000);
    BCIN = $urandom_range(0,1000);
    CARRYIN = $random;
    OPMODE = $random;
    Flag = 1;
end
$display("\n\t\t Finish Testbench With 0 Errors & 0 Design Checks\n");

$stop;
end

always @(M) begin
    M_REF = BCOUT * A;
end

// Test M & BCOUT (Depend On M as M Correct So BCOUT is Correct)
always @(negedge CLK) begin
    if (Flag) begin
        #10;
        if (M != M_REF) begin
            $display("The DSP Design is Wrong !");
            $stop;
        end
    end
end

// Test P & PCOUT (Depend On P as P is Correct So PCOUT is Correct) & CARRYOUT & CARRYOUTF
always @(negedge CLK) begin
    if (Flag) begin
        #10;
        // Test P & CARRYOUT When Out of X_MUX = M & Z_MUX = 0
        if ((OPMODE[1:0] == 2'b01) && (OPMODE[3:2] == 2'b00)) begin
            if ((P != M) && (CARRYOUT != 0)) begin
                $display("The DSP Design is Wrong !");
                $stop;
            end
        end
    end
end

initial
$monitor("Time = %0t,A = %d,B = %d,C = %d,D = %d,OPMODE = %b,M = %d,Mref = %d,
        BCOUT = %d", $time,A,B,C,D,OPMODE,M,M_REF,BCOUT);

endmodule

```



DO FILE

```
vlib work  
  
vlog DSP48A1.v Comb_Seq_MUX.v DSP48A1_tb.v  
  
vsim -voptargs = +acc work.DSP48A1_tb  
  
add wave *  
  
run -all
```



Questa Sim

WAVEFORM

  


MONITOR

```

# Time = 0, A = 0, B = 0, C = 0, D = 0, OPMODE = 00000000, M = x, Mref = x, BCOUT = x
# Time = 1, A = 0, B = 0, C = 0, D = 0, OPMODE = 00000000, M = 0, Mref = 0, BCOUT = 0
# Time = 42, A = 188, B = 844, C = 555, D = 48, OPMODE = 10000001, M = 0, Mref = 0, BCOUT = 0
# Time = 43, A = 188, B = 844, C = 555, D = 48, OPMODE = 10000001, M = 0, Mref = 0, BCOUT = 844
# Time = 45, A = 188, B = 844, C = 555, D = 48, OPMODE = 10000001, M = 158672, Mref = 158672, BCOUT = 844
# Time = 52, A = 539, B = 930, C = 880, D = 868, OPMODE = 01100011, M = 158672, Mref = 158672, BCOUT = 844
# Time = 53, A = 539, B = 930, C = 880, D = 868, OPMODE = 01100011, M = 158672, Mref = 158672, BCOUT = 930
# Time = 55, A = 539, B = 930, C = 880, D = 868, OPMODE = 01100011, M = 501270, Mref = 501270, BCOUT = 930
# Time = 62, A = 82, B = 189, C = 619, D = 409, OPMODE = 10001101, M = 501270, Mref = 501270, BCOUT = 930
# Time = 63, A = 82, B = 189, C = 619, D = 409, OPMODE = 10001101, M = 501270, Mref = 501270, BCOUT = 189
# Time = 65, A = 82, B = 189, C = 619, D = 409, OPMODE = 10001101, M = 15498, Mref = 15498, BCOUT = 189
# Time = 72, A = 664, B = 846, C = 502, D = 288, OPMODE = 00010010, M = 15498, Mref = 15498, BCOUT = 189
# Time = 73, A = 664, B = 846, C = 502, D = 288, OPMODE = 00010010, M = 15498, Mref = 15498, BCOUT = 846
# Time = 75, A = 664, B = 846, C = 502, D = 288, OPMODE = 00010010, M = 561744, Mref = 752976, BCOUT = 1134
# Time = 77, A = 664, B = 846, C = 502, D = 288, OPMODE = 00010010, M = 752976, Mref = 752976, BCOUT = 1134
# Time = 82, A = 667, B = 820, C = 103, D = 837, OPMODE = 00001101, M = 752976, Mref = 752976, BCOUT = 1134
# Time = 83, A = 667, B = 820, C = 103, D = 837, OPMODE = 00001101, M = 752976, Mref = 752976, BCOUT = 1108
# Time = 85, A = 667, B = 820, C = 103, D = 837, OPMODE = 00001101, M = 739036, Mref = 546940, BCOUT = 820
# Time = 87, A = 667, B = 820, C = 103, D = 837, OPMODE = 00001101, M = 546940, Mref = 546940, BCOUT = 820
# Time = 92, A = 928, B = 803, C = 138, D = 943, OPMODE = 00111101, M = 546940, Mref = 546940, BCOUT = 820
# Time = 93, A = 928, B = 803, C = 138, D = 943, OPMODE = 00111101, M = 546940, Mref = 546940, BCOUT = 803
# Time = 95, A = 928, B = 803, C = 138, D = 943, OPMODE = 00111101, M = 745184, Mref = 1620288, BCOUT = 1746
# Time = 97, A = 928, B = 803, C = 138, D = 943, OPMODE = 00111101, M = 1620288, Mref = 1620288, BCOUT = 1746
# Time = 102, A = 271, B = 182, C = 847, D = 369, OPMODE = 10001100, M = 1620288, Mref = 1620288, BCOUT = 1746
# Time = 103, A = 271, B = 182, C = 847, D = 369, OPMODE = 10001100, M = 1620288, Mref = 1620288, BCOUT = 1125
# Time = 105, A = 271, B = 182, C = 847, D = 369, OPMODE = 10001100, M = 304875, Mref = 49322, BCOUT = 182
# Time = 107, A = 271, B = 182, C = 847, D = 369, OPMODE = 10001100, M = 49322, Mref = 49322, BCOUT = 182
# Time = 112, A = 671, B = 567, C = 814, D = 706, OPMODE = 11000110, M = 49322, Mref = 49322, BCOUT = 182
# Time = 113, A = 671, B = 567, C = 814, D = 706, OPMODE = 11000110, M = 49322, Mref = 49322, BCOUT = 567
# Time = 115, A = 671, B = 567, C = 814, D = 706, OPMODE = 11000110, M = 380457, Mref = 380457, BCOUT = 567
# Time = 122, A = 213, B = 936, C = 138, D = 731, OPMODE = 10101010, M = 380457, Mref = 380457, BCOUT = 567
# Time = 123, A = 213, B = 936, C = 138, D = 731, OPMODE = 10101010, M = 380457, Mref = 380457, BCOUT = 936
# Time = 125, A = 213, B = 936, C = 138, D = 731, OPMODE = 10101010, M = 199368, Mref = 199368, BCOUT = 936
# Time = 132, A = 769, B = 967, C = 197, D = 541, OPMODE = 01110111, M = 199368, Mref = 199368, BCOUT = 936
# Time = 133, A = 769, B = 967, C = 197, D = 541, OPMODE = 01110111, M = 199368, Mref = 199368, BCOUT = 967
# Time = 135, A = 769, B = 967, C = 197, D = 541, OPMODE = 01110111, M = 743623, Mref = 201261142, BCOUT = 261718
# Time = 137, A = 769, B = 967, C = 197, D = 541, OPMODE = 01110111, M = 201261142, Mref = 201261142, BCOUT = 261718
# Time = 142, A = 204, B = 291, C = 737, D = 462, OPMODE = 10001111, M = 201261142, Mref = 201261142, BCOUT = 261718
# Time = 143, A = 204, B = 291, C = 737, D = 462, OPMODE = 10001111, M = 201261142, Mref = 201261142, BCOUT = 250
# Time = 145, A = 204, B = 291, C = 737, D = 462, OPMODE = 10001111, M = 51000, Mref = 59364, BCOUT = 291
# Time = 147, A = 204, B = 291, C = 737, D = 462, OPMODE = 10001111, M = 59364, Mref = 59364, BCOUT = 291
# Time = 152, A = 957, B = 49, C = 812, D = 661, OPMODE = 11001110, M = 59364, Mref = 59364, BCOUT = 291
# Time = 153, A = 957, B = 49, C = 812, D = 661, OPMODE = 11001110, M = 59364, Mref = 59364, BCOUT = 49
# Time = 155, A = 957, B = 49, C = 812, D = 661, OPMODE = 11001110, M = 46893, Mref = 46893, BCOUT = 49
# Time = 162, A = 375, B = 763, C = 733, D = 84, OPMODE = 11000101, M = 46893, Mref = 46893, BCOUT = 49
# Time = 163, A = 375, B = 763, C = 733, D = 84, OPMODE = 11000101, M = 46893, Mref = 46893, BCOUT = 763
# Time = 165, A = 375, B = 763, C = 733, D = 84, OPMODE = 11000101, M = 286125, Mref = 286125, BCOUT = 763
# Time = 172, A = 495, B = 325, C = 497, D = 110, OPMODE = 10111101, M = 286125, Mref = 286125, BCOUT = 763
# Time = 173, A = 495, B = 325, C = 497, D = 110, OPMODE = 10111101, M = 286125, Mref = 286125, BCOUT = 325
# Time = 175, A = 495, B = 325, C = 497, D = 110, OPMODE = 10111101, M = 160875, Mref = 215325, BCOUT = 435
# Time = 177, A = 495, B = 325, C = 497, D = 110, OPMODE = 10111101, M = 215325, Mref = 215325, BCOUT = 435
# Time = 182, A = 274, B = 342, C = 329, D = 285, OPMODE = 01100101, M = 215325, Mref = 215325, BCOUT = 435
# Time = 183, A = 274, B = 342, C = 329, D = 285, OPMODE = 01100101, M = 215325, Mref = 215325, BCOUT = 452
# Time = 185, A = 274, B = 342, C = 329, D = 285, OPMODE = 01100101, M = 123848, Mref = 93708, BCOUT = 342
# Time = 187, A = 274, B = 342, C = 329, D = 285, OPMODE = 01100101, M = 93708, Mref = 93708, BCOUT = 342
# Time = 192, A = 183, B = 540, C = 934, D = 138, OPMODE = 00001010, M = 93708, Mref = 93708, BCOUT = 342
# Time = 193, A = 183, B = 540, C = 934, D = 138, OPMODE = 00001010, M = 93708, Mref = 93708, BCOUT = 540
# Time = 195, A = 183, B = 540, C = 934, D = 138, OPMODE = 00001010, M = 98820, Mref = 98820, BCOUT = 540
# Time = 202, A = 240, B = 967, C = 38, D = 473, OPMODE = 00100000, M = 98820, Mref = 98820, BCOUT = 540
# Time = 203, A = 240, B = 967, C = 38, D = 473, OPMODE = 00100000, M = 98820, Mref = 98820, BCOUT = 967
# Time = 205, A = 240, B = 967, C = 38, D = 473, OPMODE = 00100000, M = 232080, Mref = 232080, BCOUT = 967
# Time = 212, A = 425, B = 288, C = 538, D = 561, OPMODE = 10011101, M = 232080, Mref = 232080, BCOUT = 967
# Time = 213, A = 425, B = 288, C = 538, D = 561, OPMODE = 10011101, M = 232080, Mref = 232080, BCOUT = 288
# Time = 215, A = 425, B = 288, C = 538, D = 561, OPMODE = 10011101, M = 122400, Mref = 360825, BCOUT = 849
# Time = 217, A = 425, B = 288, C = 538, D = 561, OPMODE = 10011101, M = 360825, Mref = 360825, BCOUT = 849
# Time = 222, A = 860, B = 559, C = 165, D = 858, OPMODE = 00010011, M = 360825, Mref = 360825, BCOUT = 849
# Time = 223, A = 860, B = 559, C = 165, D = 858, OPMODE = 00010011, M = 360825, Mref = 360825, BCOUT = 1120
# Time = 225, A = 860, B = 559, C = 165, D = 858, OPMODE = 00010011, M = 963200, Mref = 1218620, BCOUT = 1417
# Time = 227, A = 860, B = 559, C = 165, D = 858, OPMODE = 00010011, M = 1218620, Mref = 1218620, BCOUT = 1417
#
# Finish Testbench With 0 Errors & 0 Design Checks
#

```


SCHEMATIC

 

MESSAGES


☐ Warning (91)
 ☐ Info (218)
 ☐ Status (381)
 Show All

☒ Elaborated Design (20 warnings)
 ☒ General Messages (20 warnings)

- ☒ [Synth 8-2490] overwriting previous definition of module DSP48A1 [DSP48A1.v:1]
- ☒ [Synth 8-3331] design DSP48A1 has unconnected port CARRYIN (18 more like this)
 - ☒ [Synth 8-3331] design DSP48A1 has unconnected port BCIN[17]
 - ☒ [Synth 8-3331] design DSP48A1 has unconnected port BCIN[16]
 - ☒ [Synth 8-3331] design DSP48A1 has unconnected port BCIN[15]
 - ☒ [Synth 8-3331] design DSP48A1 has unconnected port BCIN[14]
 - ☒ [Synth 8-3331] design DSP48A1 has unconnected port BCIN[13]
 - ☒ [Synth 8-3331] design DSP48A1 has unconnected port BCIN[12]
 - ☒ [Synth 8-3331] design DSP48A1 has unconnected port BCIN[11]
 - ☒ [Synth 8-3331] design DSP48A1 has unconnected port BCIN[10]
 - ☒ [Synth 8-3331] design DSP48A1 has unconnected port BCIN[9]
 - ☒ [Synth 8-3331] design DSP48A1 has unconnected port BCIN[8]
 - ☒ [Synth 8-3331] design DSP48A1 has unconnected port BCIN[7]
 - ☒ [Synth 8-3331] design DSP48A1 has unconnected port BCIN[6]
 - ☒ [Synth 8-3331] design DSP48A1 has unconnected port BCIN[5]
 - ☒ [Synth 8-3331] design DSP48A1 has unconnected port BCIN[4]
 - ☒ [Synth 8-3331] design DSP48A1 has unconnected port BCIN[3]
 - ☒ [Synth 8-3331] design DSP48A1 has unconnected port BCIN[2]
 - ☒ [Synth 8-3331] design DSP48A1 has unconnected port BCIN[1]
 - ☒ [Synth 8-3331] design DSP48A1 has unconnected port BCIN[0]
- ☒ Synthesis (58 warnings)

Synthesis


SCHEMATIC

 


UTILIZATION

Summary

Resource	Utilization	Available	Utilization %
LUT	255	134600	0.19
FF	160	269200	0.06
DSP	1	740	0.14
IO	327	500	65.40

 

The Linter

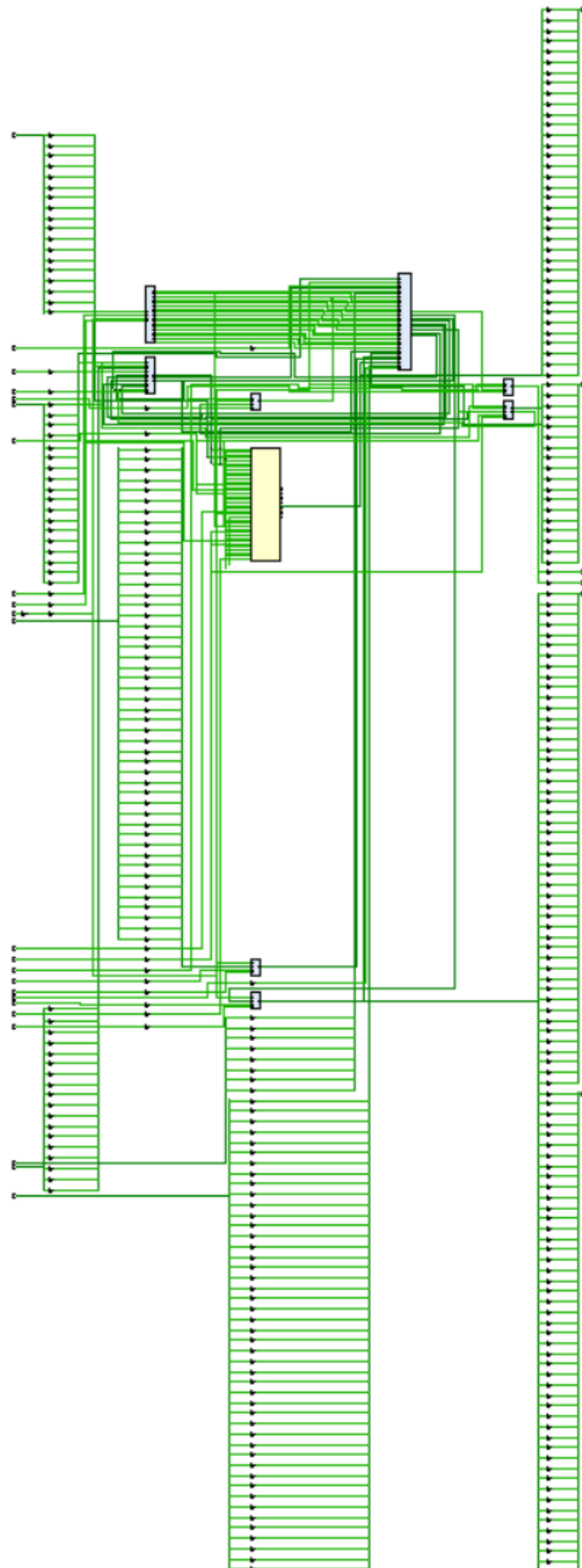

MESSAGES

▼ Synthesis (58 warnings)

1 [Synth 8-2490] overwriting previous definition of module DSP48A1 [DSP48A1.v:1]

▼ 1 [Synth 8-3331] design DSP48A1 has unconnected port CARRYIN (37 more like this)

- 1 [Synth 8-3331] design DSP48A1 has unconnected port BCIN[17]
- 1 [Synth 8-3331] design DSP48A1 has unconnected port BCIN[16]
- 1 [Synth 8-3331] design DSP48A1 has unconnected port BCIN[15]
- 1 [Synth 8-3331] design DSP48A1 has unconnected port BCIN[14]
- 1 [Synth 8-3331] design DSP48A1 has unconnected port BCIN[13]
- 1 [Synth 8-3331] design DSP48A1 has unconnected port BCIN[12]
- 1 [Synth 8-3331] design DSP48A1 has unconnected port BCIN[11]
- 1 [Synth 8-3331] design DSP48A1 has unconnected port BCIN[10]
- 1 [Synth 8-3331] design DSP48A1 has unconnected port BCIN[9]
- 1 [Synth 8-3331] design DSP48A1 has unconnected port BCIN[8]
- 1 [Synth 8-3331] design DSP48A1 has unconnected port BCIN[7]
- 1 [Synth 8-3331] design DSP48A1 has unconnected port BCIN[6]
- 1 [Synth 8-3331] design DSP48A1 has unconnected port BCIN[5]
- 1 [Synth 8-3331] design DSP48A1 has unconnected port BCIN[4]
- 1 [Synth 8-3331] design DSP48A1 has unconnected port BCIN[3]
- 1 [Synth 8-3331] design DSP48A1 has unconnected port BCIN[2]
- 1 [Synth 8-3331] design DSP48A1 has unconnected port BCIN[1]
- 1 [Synth 8-3331] design DSP48A1 has unconnected port BCIN[0]
- 1 [Synth 8-3331] design DSP48A1 has unconnected port CARRYIN
- 1 [Synth 8-3331] design DSP48A1 has unconnected port BCIN[17]
- 1 [Synth 8-3331] design DSP48A1 has unconnected port BCIN[16]
- 1 [Synth 8-3331] design DSP48A1 has unconnected port BCIN[15]
- 1 [Synth 8-3331] design DSP48A1 has unconnected port BCIN[14]
- 1 [Synth 8-3331] design DSP48A1 has unconnected port BCIN[13]
- 1 [Synth 8-3331] design DSP48A1 has unconnected port BCIN[12]
- 1 [Synth 8-3331] design DSP48A1 has unconnected port BCIN[11]
- 1 [Synth 8-3331] design DSP48A1 has unconnected port BCIN[10]
- 1 [Synth 8-3331] design DSP48A1 has unconnected port BCIN[9]
- 1 [Synth 8-3331] design DSP48A1 has unconnected port BCIN[8]
- 1 [Synth 8-3331] design DSP48A1 has unconnected port BCIN[7]
- 1 [Synth 8-3331] design DSP48A1 has unconnected port BCIN[6]
- 1 [Synth 8-3331] design DSP48A1 has unconnected port BCIN[5]
- 1 [Synth 8-3331] design DSP48A1 has unconnected port BCIN[4]
- 1 [Synth 8-3331] design DSP48A1 has unconnected port BCIN[3]
- 1 [Synth 8-3331] design DSP48A1 has unconnected port BCIN[2]
- 1 [Synth 8-3331] design DSP48A1 has unconnected port BCIN[1]
- 1 [Synth 8-3331] design DSP48A1 has unconnected port BCIN[0]


> 1 [Synth 8-3332] Sequential element (B0_REG/OUT_Seq_reg[17]) is unused and will be removed from module DSP48A1. (17 more like this)

1 [Constraints 18-5210] No constraint will be written out.

> Implementation (6 warnings)

Implementation


SCHEMATIC

 


MESSAGES


- Implementation (6 warnings)
 - Opt Design (1 warning)
 - [Constraints 18-5210] No constraint will be written out.
 - Place Design (2 warnings)
 - [Place 46-29] place_design is not in timing mode. Skip physical synthesis in placer
 - [Constraints 18-5210] No constraint will be written out.
 - Route Design (3 warnings)
 - [Constraints 18-5210] No constraint will be written out.
 - [Power 33-232] No user defined clocks were found in the design!
Resolution: Please specify clocks using create_clock/create_generated_clock for sequential elements. For pure combinatorial circuits, please specify a virtual clock, otherwise the vectorless estimation might be inaccurate
 - [Timing 38-313] There are no user specified timing constraints. Timing constraints are needed for proper timing analysis.
- Implemented Design (1 warning)
 - General Messages (1 warning)
 - [Timing 38-313] There are no user specified timing constraints. Timing constraints are needed for proper timing analysis.

The Linter

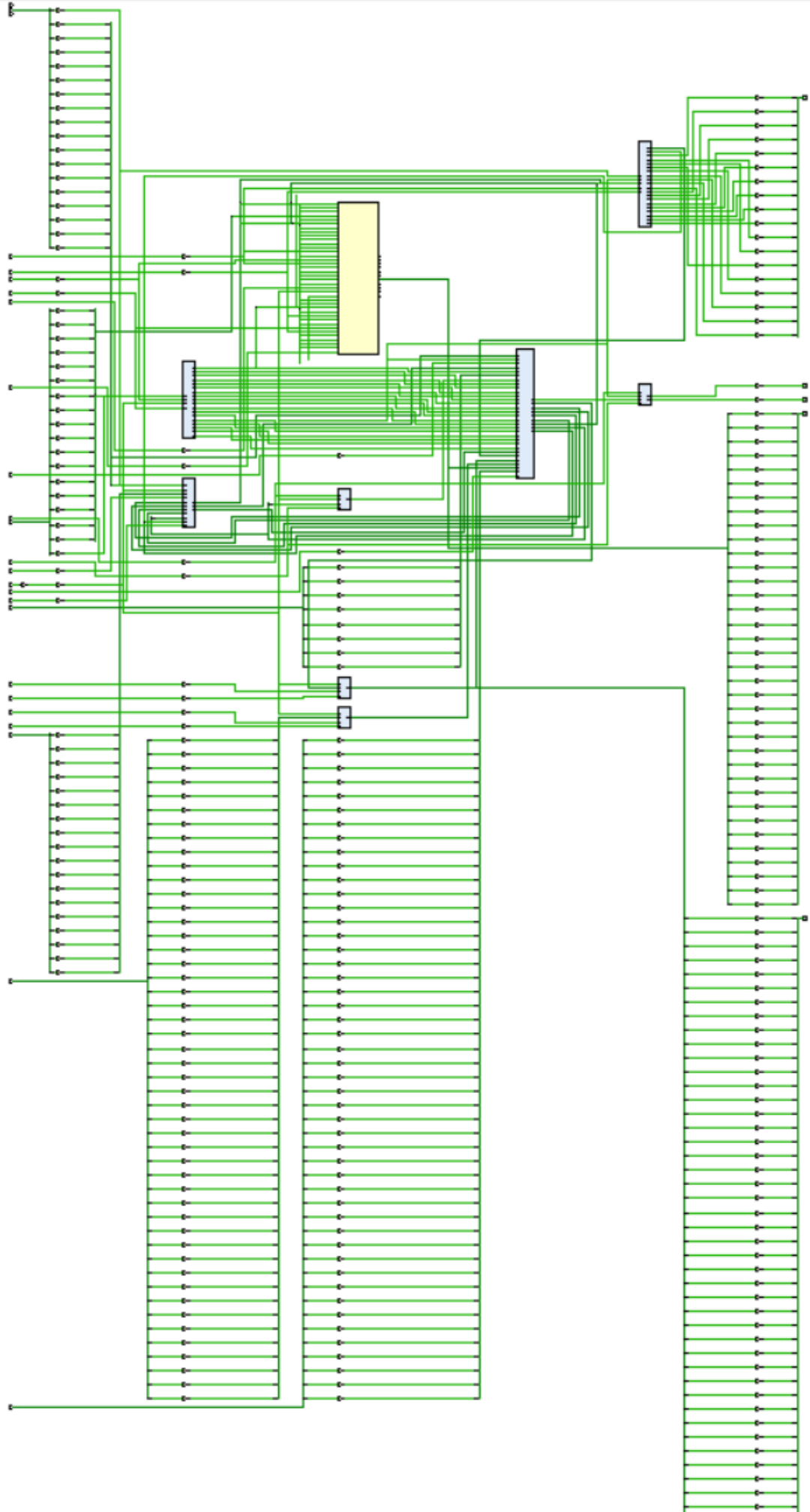

DEVICE

 


 

UTILIZATION

Summary

Resource	Utilization	Available	Utilization %
LUT	254	134600	0.19
FF	179	269200	0.07
DSP	1	740	0.14
IO	327	500	65.40

 

Summary

Power analysis from Implemented netlist. Activity derived from constraints files, simulation files or vectorless analysis.

Total On-Chip Power: **135.651 W (Junction temp exceeded!)**
Design Power Budget: **Not Specified**
Power Budget Margin: **N/A**
Junction Temperature: **125.0°C**
Thermal Margin: **-136.7°C (-93.1 W)**
Effective θ_{JA} : **1.5°C/W**
Power supplied to off-chip devices: **0 W**
Confidence level: **Low**

[Launch Power Constraint Advisor](#) to find and fix invalid switching activity

On-Chip Power

